

PEE ACTIVITIES FROM MONDAY 16 TO MONDAY 23.

1.- Access to the Yenka website to download the program.

2.- Try to assemble the following circuits:

2.1.- A circuit that activates an alarm when the temperature in a room became too high.

2.2.- A circuit that activates an alarm when the humidity in a room became too high.

3.- Remember that you can ask me your questions on irene.profeinformatica@yahoo.es